

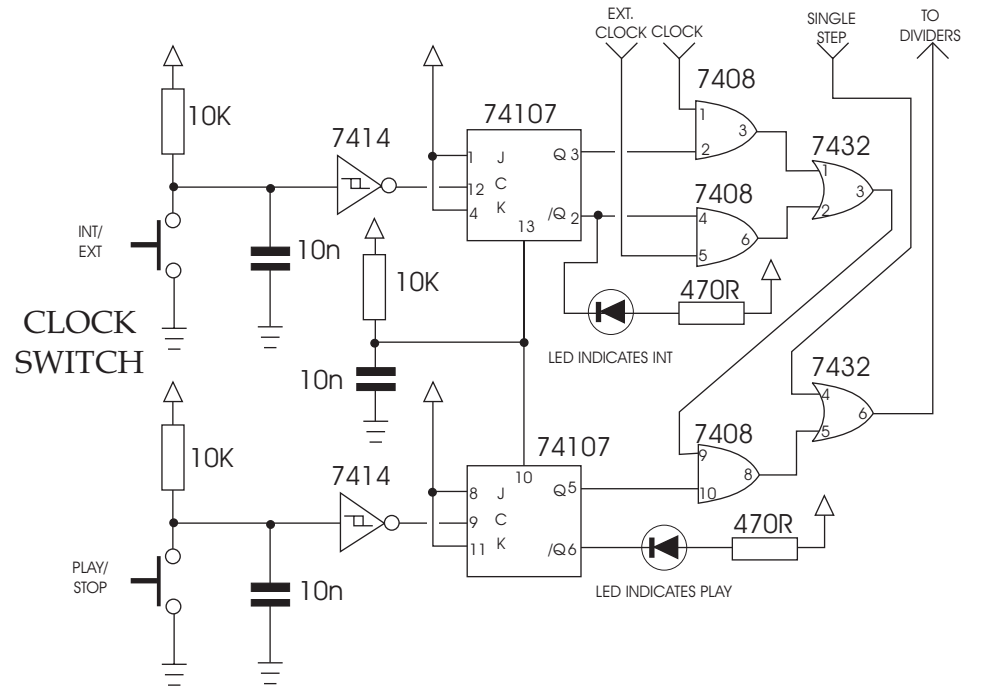
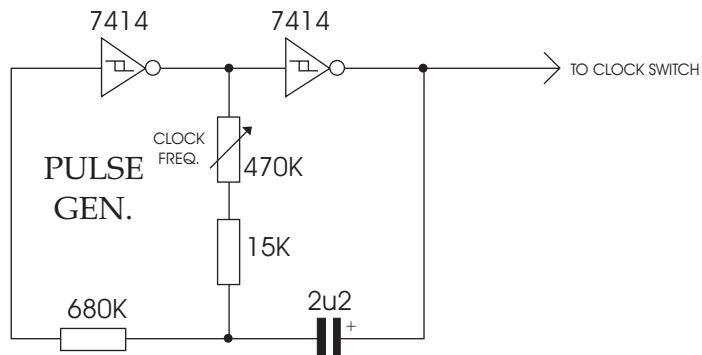
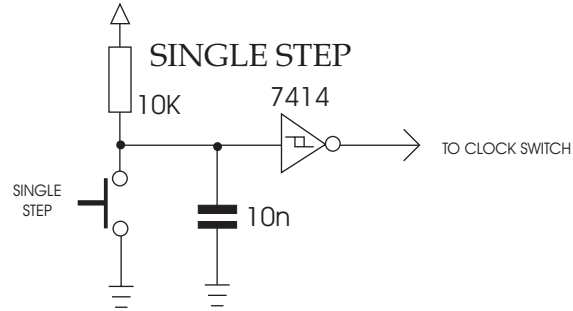



# The Simple Sequencer

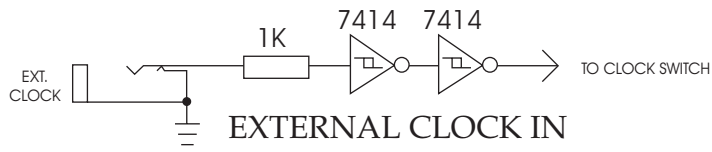

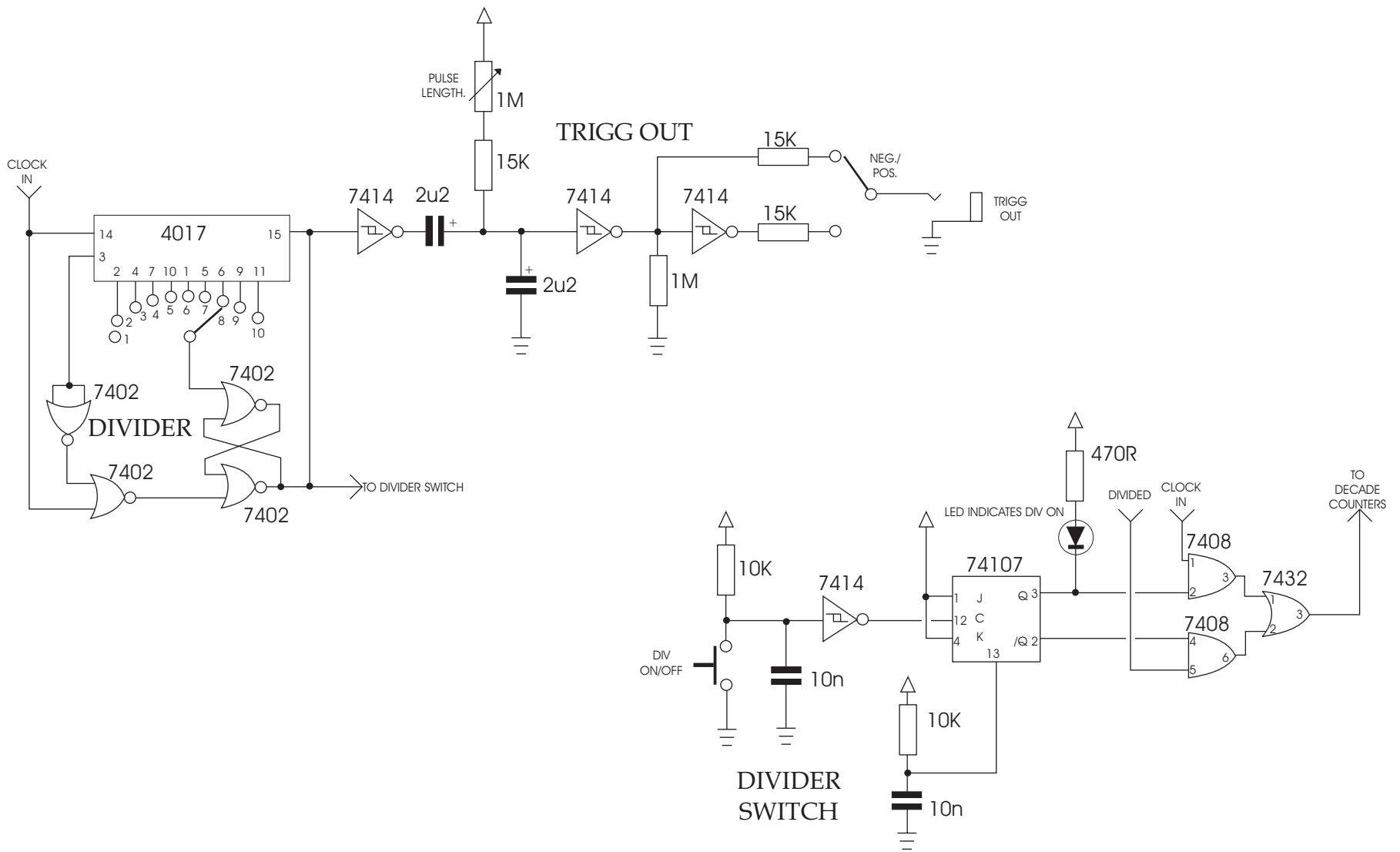
**Schematics 1**  
 External clock in, Pulse (Clock) generator,  
 Single step, Clock switch




**Schematics 2** (2 of each - A & B)  
 Divider, Trigg out, Divider switch  
 LED indicates when Divider is used.

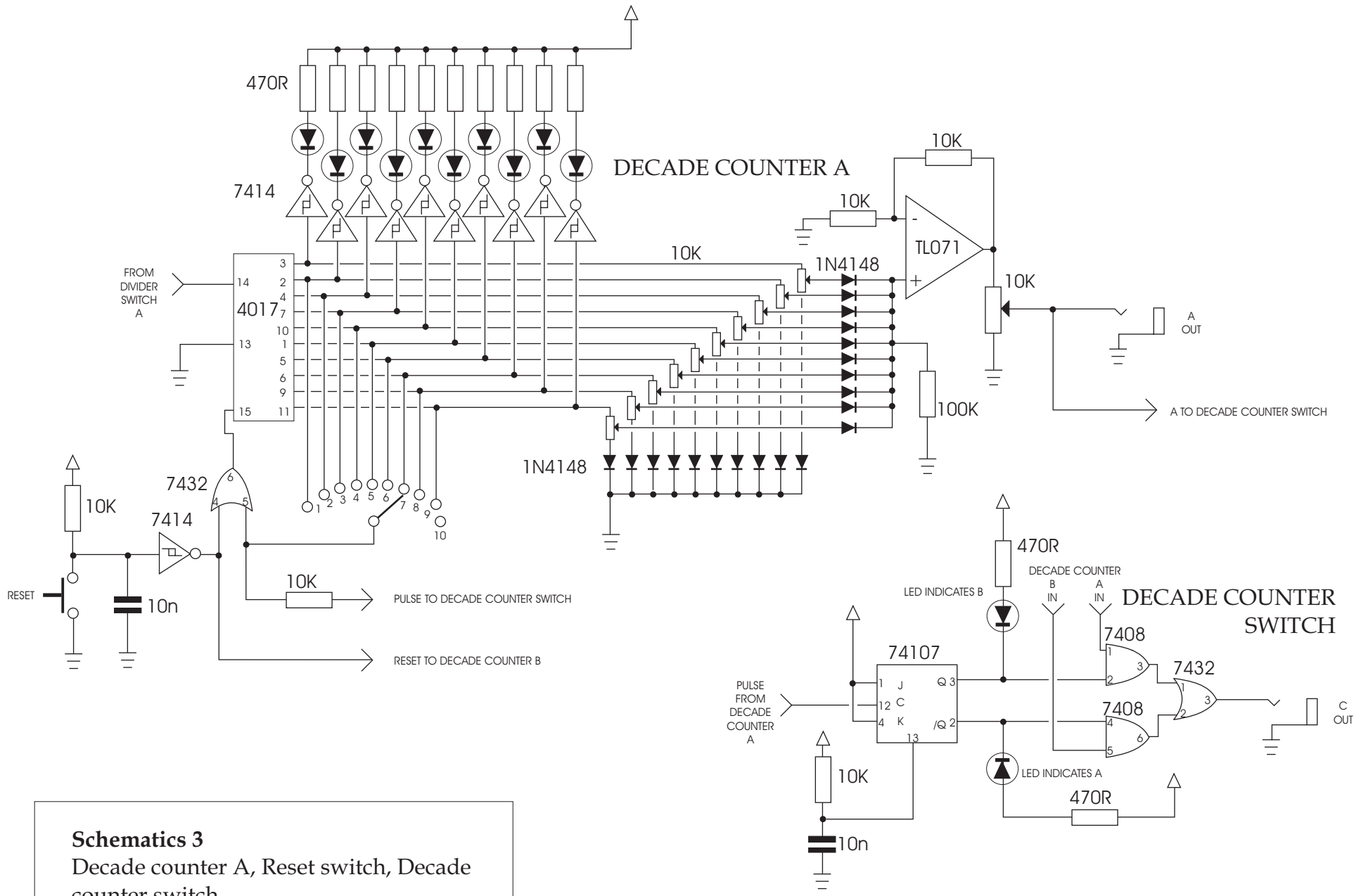

**Schematics 3**  
Decade counter A, Reset switch, Decade counter switch

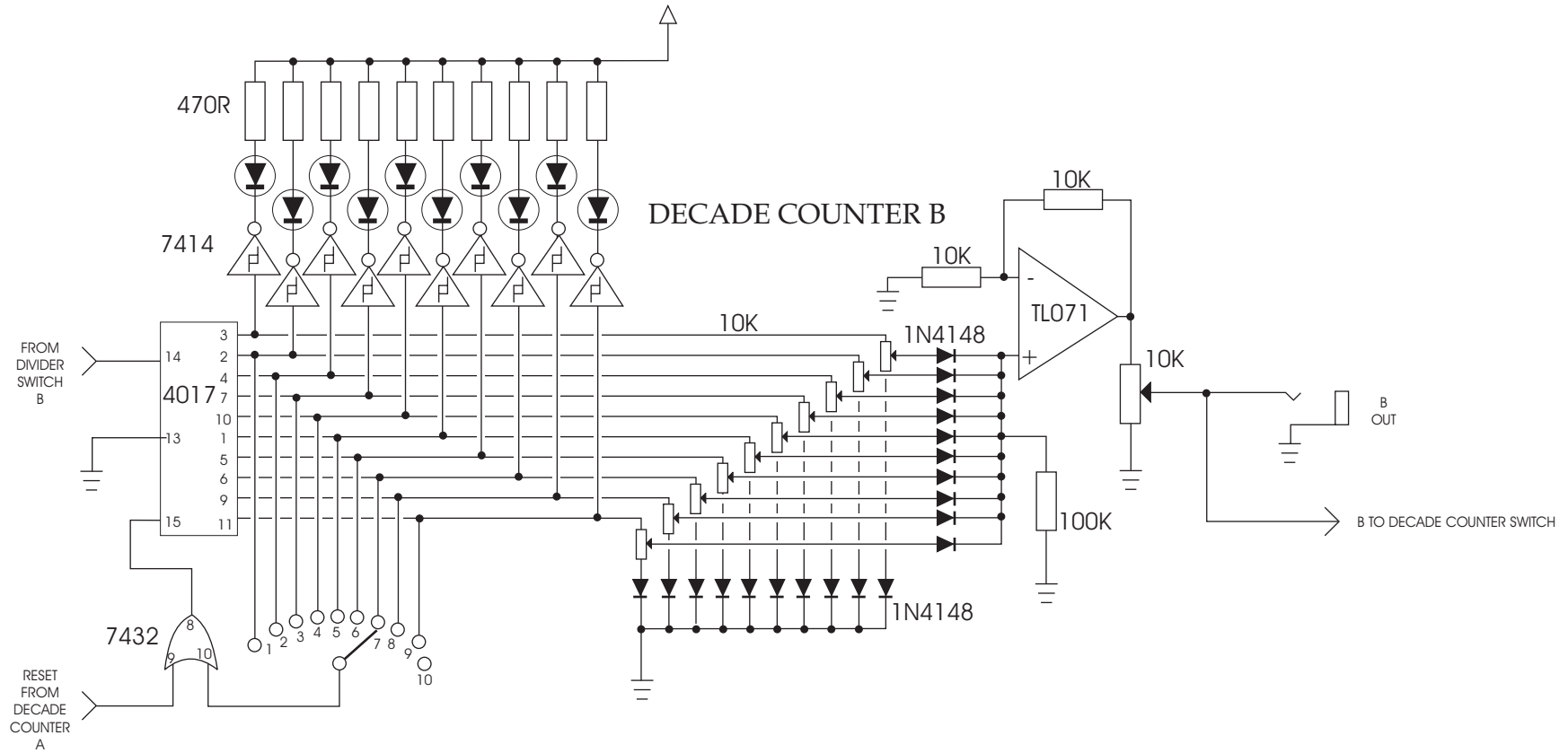

**Schematics 4**  
 Decade counter B

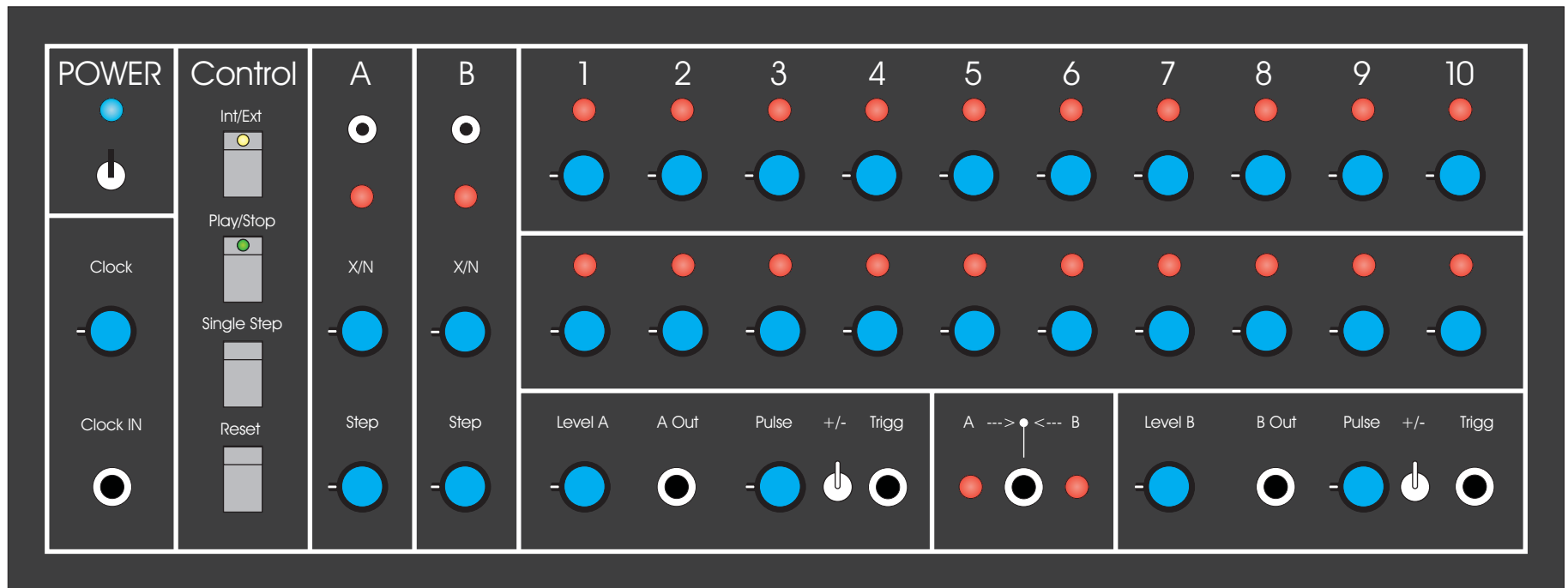


**Layout**  
The Simple Sequencer (60%)


### PCB 1 (35x130)

Switch board. Internal/External clock,  
Play/Stop, Single Step, Reset

#### Parts placing

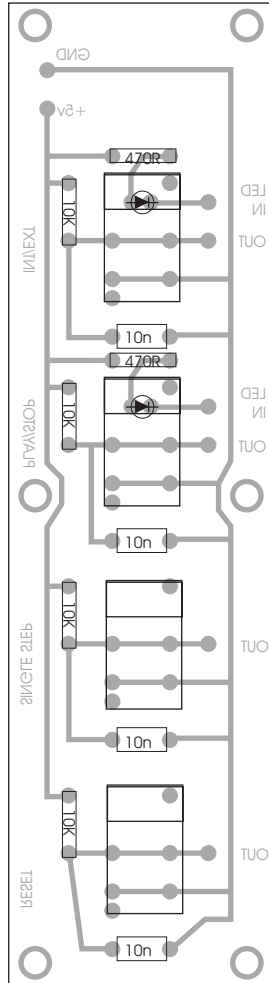


#### PCB (35x130)

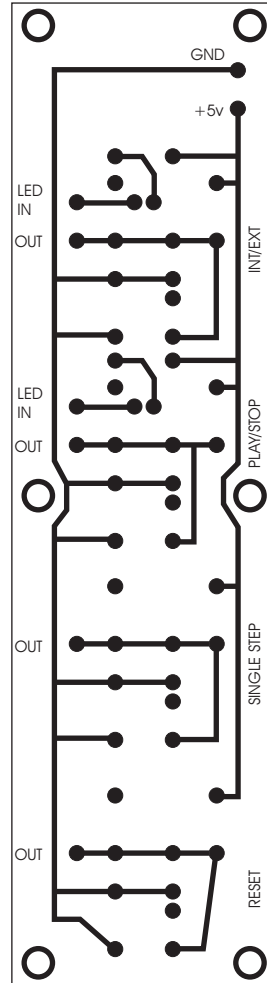


# PCB2 (120x80)

Step 1 to 5, channel A and B

## Parts placing

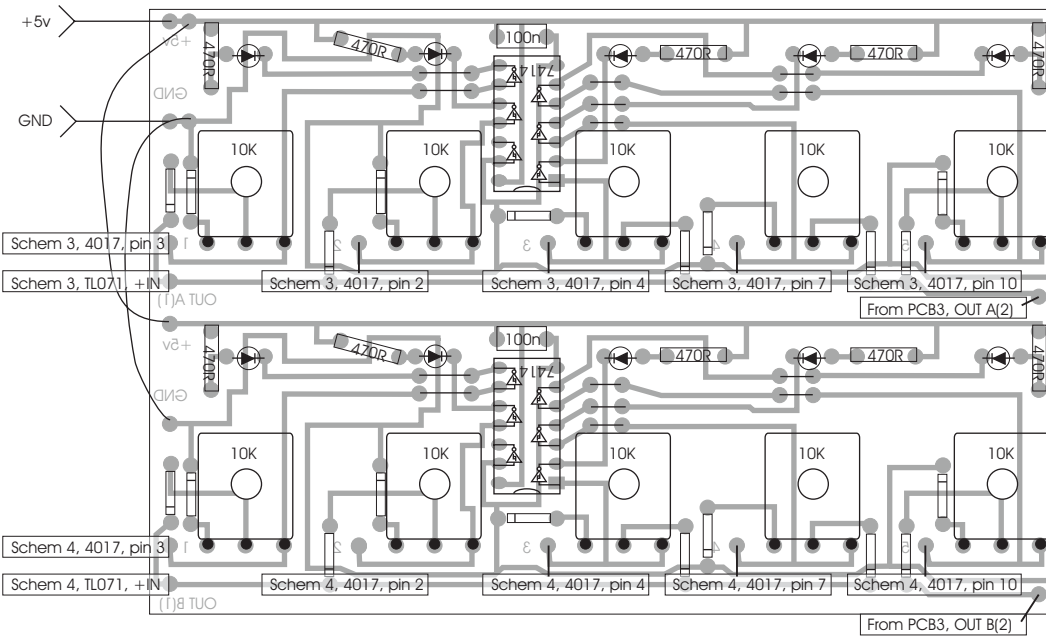

## PCB (120x80)


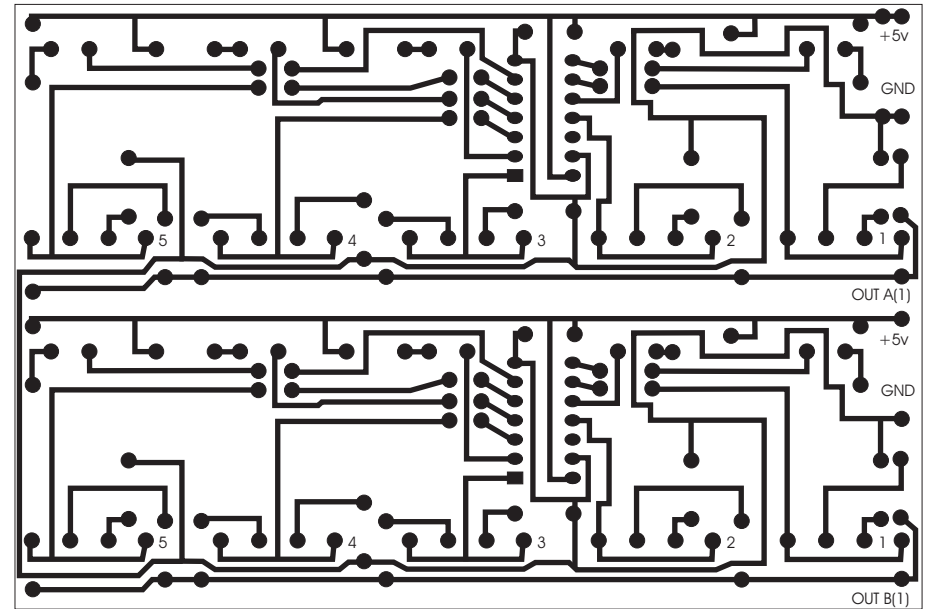


# PCB3 (120x80)

Step 6 to 10, channel A and B

## Parts placing


## PCB (120x80)

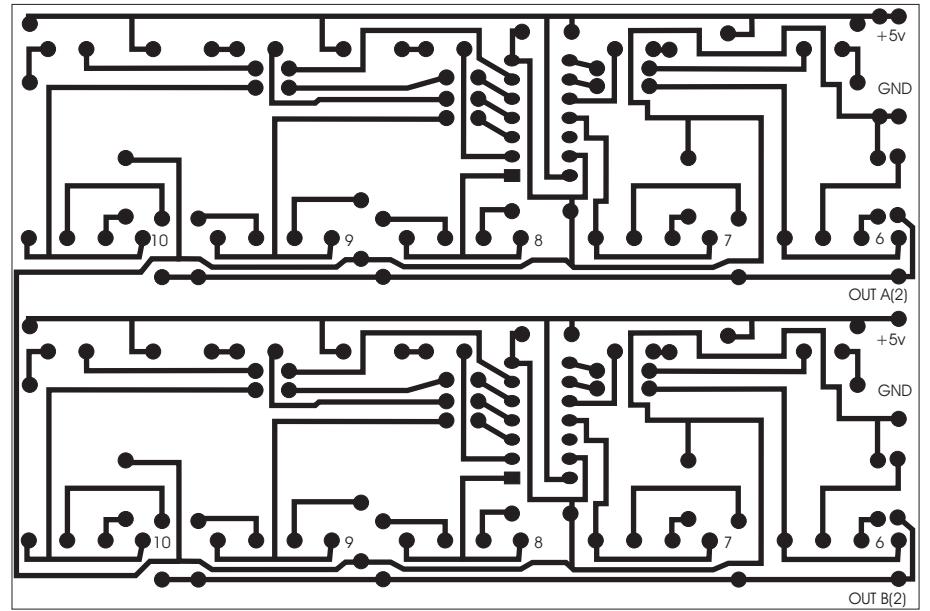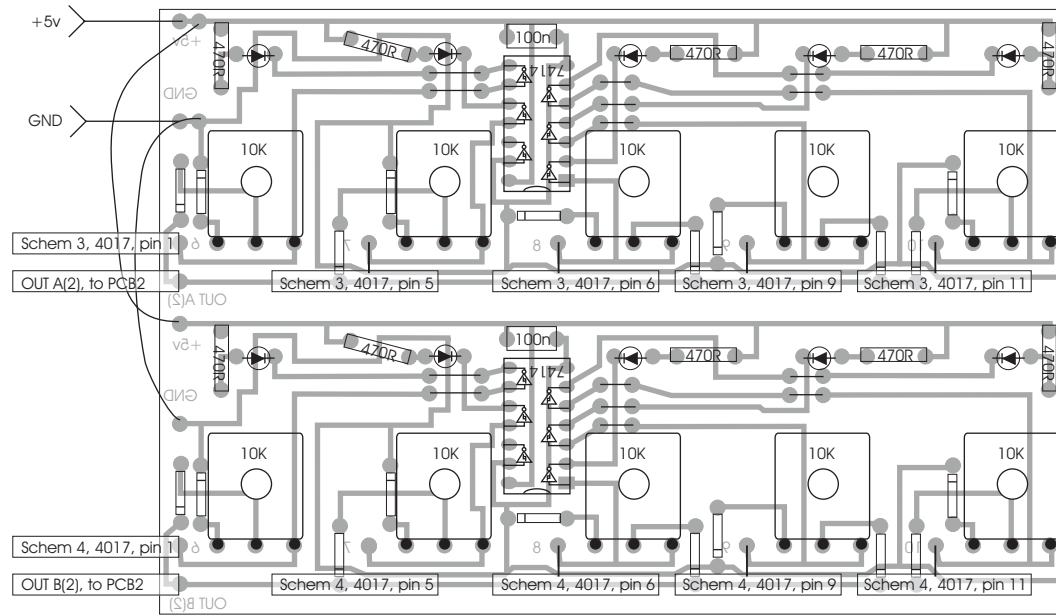


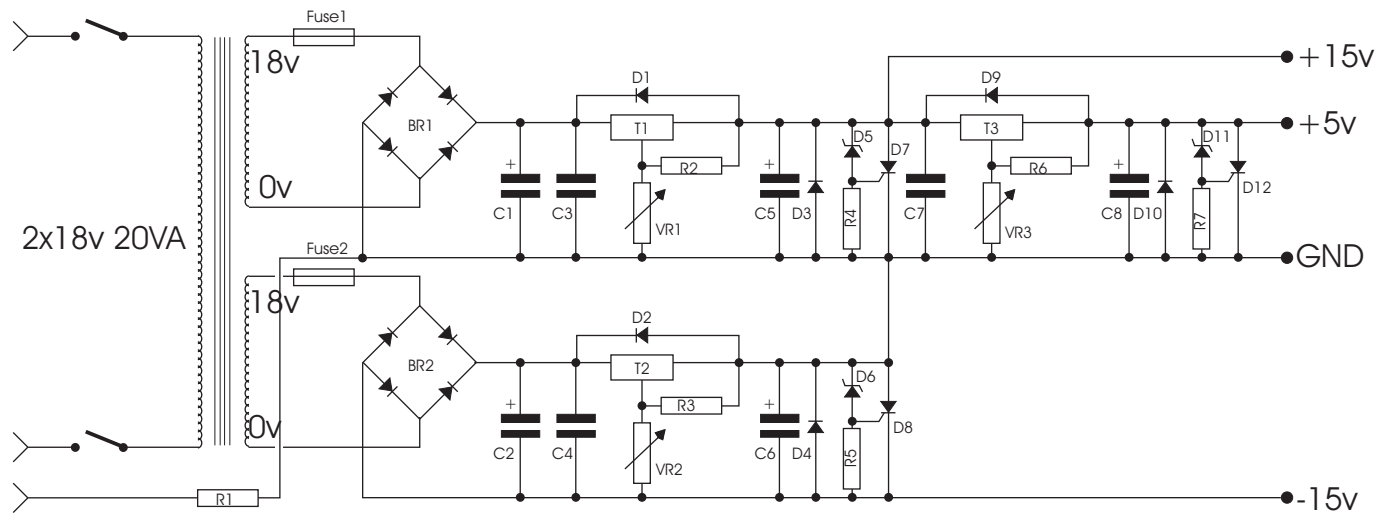
## PSU Schematic

Decade counter A, Decade counter B  
Decade counter switch




### Parts list


R1 = 330R  
R2, R3 = 450R  
R4, R5, R7 = 33R  
R6 = 1.6k  
VR1, VR2, VR3 = 10k

C1, C2 = 2200uF  
C3, C4, C7 = 100nF  
C5, C6, C8 = 22uF  
D1, D2, D3, D4, D9, D10 = 1N4001  
D5, D6 = 16v zener

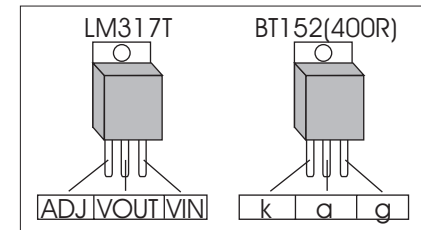D11 = 5.6v zener  
D7, D8, D12 = BT152 400R  
BR1, BR2 = KBP204G  
T1, T2, T3 = LM317T  
Fuse1, Fuse2 = 1.0 A



**PCB5 (85x105)**  
PSU

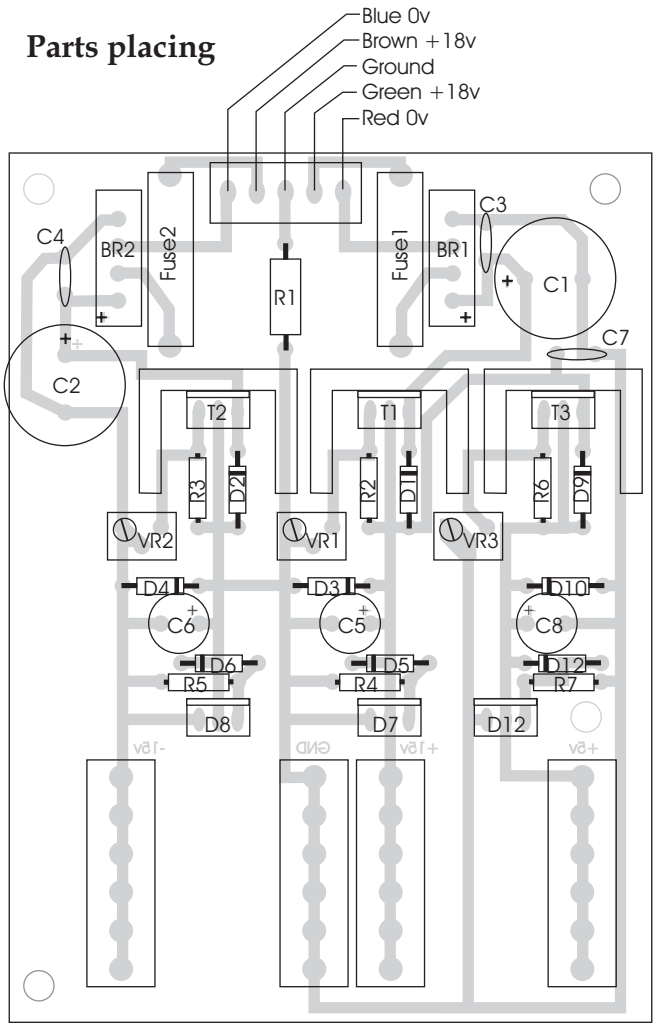

**PCB 85x105**

